

Keywords: analog filter, microprocessor supervisor, uP supervisor, reset circuit, power fail comparator

APPLICATION NOTE 23

μP-Supervisor Chip Controls Programmable Filter

Jul 09, 1998

Abstract: An application showing how the use of a microprocessor supervisor can be used to program a dual section filter. Using the time delay from the reset circuit and strapping it to the power-fail comparator with a delay circuit, the filter can easily be programmed to provide the correct cutoff frequencies during power up using this reset circuit.

Certain dual-section filter ICs have a common 7-bit port for programming the two cutoff frequencies (f_C). If both sections require the same f_C , you can strap an appropriate code to the port pins, but other applications require a different f_C for each section. In such cases, a microprocessor is the obvious tool for sequentially programming the two filter sections, but lacking a μP , you can do the job without the circuit of **Figure 1**.

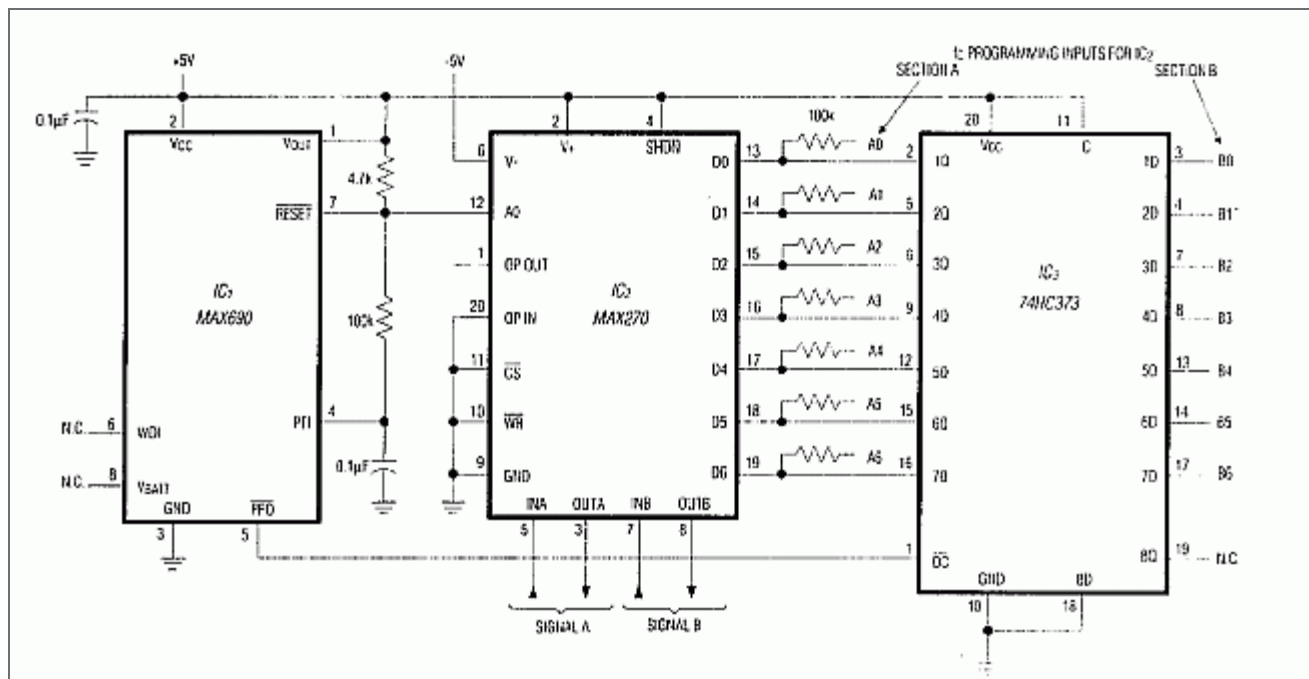


Figure 1. A μP -supervisory chip (IC1) directs the sequential loading of f_C data into the dual, programmable lowpass filter IC2. The circuit reloads this f_C data following each power-up.

IC₂ is a continuous, dual-lowpass filter containing identical 2nd-order sections A and B. To program desired f_C values, obtain corresponding codes from the data sheet and connect each pin of A0-A6 and B0-B6 to 5V ("1") or GND ("0") accordingly. (The latches internal to inputs D0-D6 remain "transparent" because inputs active-low)

WR and active-low CS are wired low.)

Latch IC₃ also remains transparent because pin 11 is wired high. The latch outputs (1Q-7Q) are three-stated when the Output Control (active-low OC, pin 1) is driven high. When active-low OC is high, therefore, A0-A6 data drives the filter port (D0-D6). When active-low OC is low, B0-B6 data appears at the latch outputs and overrides A0-A6.

The μ P-supervisory chip IC₁, though normally used to monitor supply voltage and software execution in a μ P system, generates directly usable signals for controlling IC₂ and IC₃: active-low RESET (pin 7), which remains low for 50msec after power-up, directs the input port of IC₂ first to filter section A, then to section B. Active-low PFO (Power Fail Output, pin 5), which goes high in a few milliseconds after active-low RESET, provides a properly timed control signal for three-stating the latch outputs of IC₃ (**Figure 2**).

 


Figure 2. Timing relationships for the Figure 1 circuit.

The circuit as shown requires $\pm 5V$ supplies. To operate on $\pm 2.5V$ or on 5V alone, connect IC₁'s GND pin to the lower supply rail and drive IC₂'s pin 12 through a resistive divider (see MAX270 data sheet, Figure 3).

Related Parts

MAX270	Digitally Programmable, Dual, 2nd-Order, Continuous Lowpass Filter	Free Samples
MAX690	Microprocessor Supervisory Circuits	Free Samples

More Information

For Technical Support: <http://www.maximintegrated.com/support>

For Samples: <http://www.maximintegrated.com/samples>

Other Questions and Comments: <http://www.maximintegrated.com/contact>

Application Note 23: <http://www.maximintegrated.com/an23>

APPLICATION NOTE 23, AN23, AN 23, APP23, Appnote23, Appnote 23

Copyright © by Maxim Integrated Products

Additional Legal Notices: <http://www.maximintegrated.com/legal>